

No. of Printed Pages : 3

BEY-012

**BACHELOR OF SCIENCE (APPLIED
SCIENCE-ENERGY) (BSCAEY)**

Term-End Examination

December, 2024

**BEY-012 : ELECTRICAL AND ELECTRONICS
SCIENCES**

Time : 3 Hours

Maximum Marks : 70

Note : Attempt any **five** questions. All questions carry equal marks.

1. (a) Mention various advantages of electrical energy over other types of energy. 7
- (b) State and explain Faraday's law of electromagnetic induction. 7
2. (a) Write the phasor diagram for the following combination when the circuits are excited by single phase AC supply : 7
- (i) R-C series combination
- (ii) AC through pure inductive circuit

- (b) Explain the principle of operation of transformer. Draw phasor diagram of transformer on no load. 7
3. (a) The armature of 6 pole d.c. machine 0.75 metre in diameter has 664 conductors, each having an effective length of 0.30 metre and carrying a current of 100 A. If 70% of total conductors lie simultaneously in the field of average flux density of 0.85 Wb/m^2 , calculate the armature torque developed. 7

Or

Describe different interconnections and categories of DC machines.

- (b) Give the principle of operation (or working principle) of 3-phase induction motor. 7
4. (a) Explain and draw V-I relation of a diode. 7
- (b) Describe the characteristics of a transistor in CB configuration. 7
5. (a) Discuss 'NOT' and 'NOR' operations using a suitable diagram. Draw the truth table for three input 'AND' operation. 7

- (b) Explain the principle of operation of Silicon Controlled Rectifier (SCR) and draw its V-I characteristic. 7
6. (a) What is Transducer ? Give classification of transducers. 7
- (b) With the help of a block diagram, explain the functional elements of a generalised measuring system. 7
7. Write short notes on any *four* of the following :

$$4 \times 3\frac{1}{2} = 14$$

- (a) Electrical Instruments—Ammeter and voltmeter
- (b) Care and maintenance of Lead Acid Battery
- (c) Iron losses or core losses of transformer
- (d) Single-phase induction motor
- (e) Construction of a junction transistor
- (f) D and T flip-flop

× × × × × × ×