

No. of Printed Pages : 4

BEY-012

**BACHELOR OF SCIENCE (APPLIED
SCIENCE-ENERGY (BSCAEY)**

Term-End Examination

June, 2025

**BEY-012 : ELECTRICAL AND ELECTRONICS
SCIENCES**

Time : 3 Hours

Maximum Marks : 70

Note : (i) Attempt any **five** questions.

(ii) All questions carry equal marks.

-
1. (a) State and explain Kirchhoff's voltage and current law. 7
 - (b) Deduce analogy between magnetic circuit and electric circuit. What are the major points of difference between them ? 7

2. (a) Explain the phenomenon of resonance in RLC circuit. 7
- (b) Explain the construction and working principle of single phase transformer. 7
3. (a) The armature of a 8-pole d.c. generator has 960 conductors and runs at 400 r.p.m. The flux per pole is 40 MWb.
- (i) Calculate the induced e.m.f., if the armature is lap wound.
- (ii) At what speed should it be driven to generate 400 V, if the armature were wave-connected ? 7

Or

What is the basic principle of DC generator ? Write the necessary conditions for voltage buildup in a shunt generator. 7

- (b) Explain constructional features of synchronous generators. What is synchronous speed ? 7

4. (a) Explain the V-I characteristics of Zener diode and explain its working as a voltage regulator. 7

Or

Explain diode applications as rectifiers.

- (b) Describe the characteristics of a transistor in CE configuration. 7
5. (a) What is the difference between Ordinary algebra and Boolean algebra ? 7
- (b) Explain the characteristics of SCR and TRIAC. 7
6. (a) Describe functional elements of a generalized measuring system. 7
- (b) State various electrical transducers with its applications. What are the advantages of electrical transducers ? 7
7. Write short notes on any *four* of the following : $4 \times 3\frac{1}{3} = 14$
- (a) Construction of Lead Acid Battery

- (b) Energy stored in charged capacitor and inductor
- (c) Equivalent circuit of an ideal transformer
- (d) Single phase induction motor
- (e) Classification of material based on energy band theory
- (f) Active and reactive power

x x x x x