

M. SC. (PHYSICS) (MSCPH)

Term-End Examination

June, 2025

MPH-005 : ELECTRONICS

Time : 2 Hours

Maximum Marks : 50

Note : (i) Attempt any **five** questions.

(ii) You can use calculator.

(iii) Symbols have their usual meanings.

1. (a) Explain the terms forward recovery time and reverse recovery time of a power diode. 5
- (b) Differentiate between LED and Laser diode. 5

2. (a) State the advantages of JFET over BJT.

5

- (b) Draw and explain the action of CMOS inverter circuit with the help of truth table.

5

3. (a) Explain the construction and working of SCR. How does it differ from a Triac ?

4+1

- (b) In a single ended input-single ended output configuration of differential amplifier, the input voltage is 10 mV. If the collector resistors $R_{C_1} = R_{C_2} = 47\text{ k}\Omega$, emitter resistor $R_E = 39\text{ k}\Omega$ and supply voltage is $\pm 12\text{ V}$, calculate the differential gain and output voltage of the circuit. Assume Si transistors.

5

4. (a) Describe the factors giving rise to output offset voltage of op-amp. Explain the method of measuring the output resistance of the op-amp. 2+3
- (b) Design and draw the circuit of Schmitt trigger using an op-amp with hysteresis of 30% of $\pm V_{\text{Sat}}$. 5
5. State the advantages of SMPS over linear power supply. Explain with the help of appropriate diagram the working of buck converter. 3+7
6. (a) Explain the working of an astable multivibrator using an op-amp. 5
- (b) Explain the basic operation of a PLL using schematic block diagram. 5

7. (a) With the help of a block diagram, explain the working of successive approximation ADC. 7
- (b) Calculate the quantization noise of a digital signal with 20 mV step size. 3
8. (a) Draw the block diagram of the microcontroller 8051 architecture. 5
- (b) Describe the scheme used for multiplexing the address and data lines in microprocessor 8085. 5

x x x x x